


# —Chapter 8—

# **Alternating- Current Circuits**

# 8-1 Oscillator Circuit

## A. RL CIRCUIT

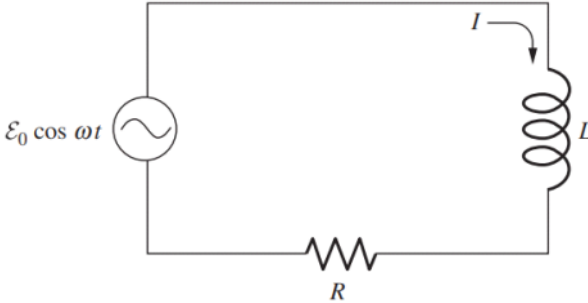- (1) A circuit with inductance, driven by an alternating electromotive force.



The Kirchhoff loop equation for the series RL circuit and the alternating current is

$$L \frac{dI}{dt} + RI = \mathcal{E}_0 \cos \omega t$$

$$I(t) = I_0 \cos(\omega t + \phi)$$

Thus, we obtain

$$-\omega LI_0 \sin(\omega t + \phi) + RI_0 \cos(\omega t + \phi) = \mathcal{E}_0 \cos \omega t \cdots \cdots (a)$$

Using trigonometric angle sum identity, we obtain

$$-\omega LI_0 (\sin \omega t \cos \phi + \cos \omega t \sin \phi)$$

$$+ RI_0 (\cos \omega t \cos \phi - \sin \omega t \sin \phi) = \mathcal{E}_0 \cos \omega t$$

$$(-\omega LI_0 \cos \phi - RI_0 \sin \phi) \sin \omega t$$

$$+ (-\omega LI_0 \sin \phi + RI_0 \cos \phi - \mathcal{E}_0) \cos \omega t = 0$$

Setting the coefficients of  $\sin \omega t$  and  $\cos \omega t$  separately equal to zero gives, respectively,

$$-\omega LI_0 \cos \phi - RI_0 \sin \phi = 0 \Rightarrow \tan \phi = -\frac{\omega L}{R}$$


and

$$-\omega LI_0 \sin \phi + RI_0 \cos \phi - \mathcal{E}_0 = 0$$

which gives

$$\begin{aligned}
 I_0 &= \frac{\mathcal{E}_0}{R \cos \phi - \omega L \sin \phi} \\
 &= \frac{\mathcal{E}_0}{R \cos \phi + R \tan \phi \sin \phi} \\
 &= \frac{\mathcal{E}_0 \cos \phi}{R(\cos^2 \phi + \sin^2 \phi)} \\
 &= \frac{\mathcal{E}_0 \cos \phi}{R}
 \end{aligned}$$

Since

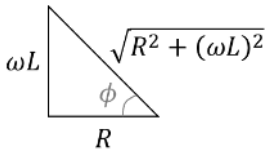

$$\cos \phi = \frac{R}{\sqrt{R^2 + (\omega L)^2}}$$


we get

$$I_0 = \frac{\mathcal{E}_0}{\sqrt{R^2 + (\omega L)^2}}$$

Since  $\omega L$  has the dimensions of resistance, this quantity is called the inductive resistance.

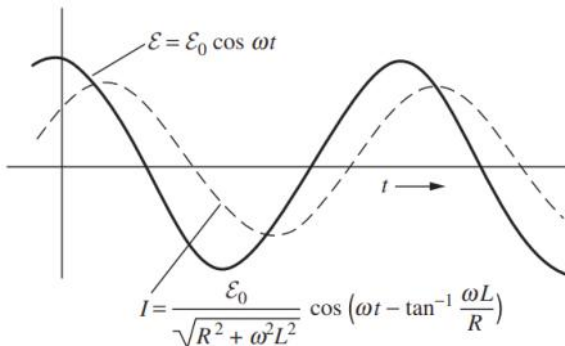(2) Thus, we have

$$\begin{aligned}
 \mathcal{E} &= \mathcal{E}_0 \cos \omega t \\
 I &= \frac{\mathcal{E}_0}{\sqrt{R^2 + (\omega L)^2}} \cos \left( \omega t - \tan^{-1} \frac{\omega L}{R} \right)
 \end{aligned}$$



Since  $\phi$  is a negative angle, the current reaches its maximum a bit later than the electromotive force.

(3) Complex exponential solutions - A powerful and beautiful method

The Kirchhoff loop equation is

$$L \frac{dI}{dt} + RI = \mathcal{E}_0 e^{i\omega t}$$

$$I(t) = \tilde{I}_0 e^{i\omega t} \text{ where } \tilde{I}_0 \text{ is a complex number}$$

Thus, we obtain

$$i\omega L \tilde{I}_0 e^{i\omega t} + R \tilde{I}_0 e^{i\omega t} = \mathcal{E}_0 e^{i\omega t}$$

Canceling the  $e^{i\omega t}$ , we get

$$\begin{aligned} \tilde{I}_0 &= \frac{\mathcal{E}_0}{i\omega L + R} \\ &= \frac{\mathcal{E}_0}{R^2 + (\omega L)^2} (R - i\omega L) \\ &= \frac{\mathcal{E}_0}{R^2 + (\omega L)^2} \sqrt{R^2 + (\omega L)^2} e^{i\phi} \\ &= \frac{\mathcal{E}_0}{\sqrt{R^2 + (\omega L)^2}} e^{i\phi} \end{aligned}$$

$$\tan \phi = -\frac{\omega L}{R} \Rightarrow \phi = \tan^{-1} \left( -\frac{\omega L}{R} \right) = -\tan^{-1} \left( \frac{\omega L}{R} \right)$$


Thus, we obtain

$$\mathcal{E} = \mathcal{E}_0 e^{i\omega t}$$

$$I = \frac{\mathcal{E}_0}{\sqrt{R^2 + (\omega L)^2}} e^{i\left(\omega t - \tan^{-1} \frac{\omega L}{R}\right)}$$

## B. RC CIRCUIT

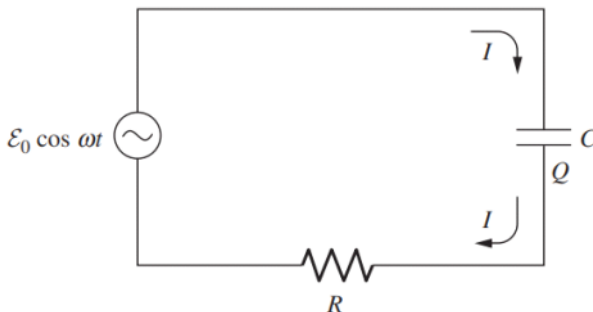- (1) An alternating electromotive force in a circuit containing resistance and capacitance where we have defined  $Q$  to be the charge on the bottom plate of the capacitor.



The Kirchhoff loop equation for the series RC circuit and the

alternating current is

$$-\frac{Q}{C} + RI = \mathcal{E}_0 e^{i\omega t}$$

$$Q = CV$$

$$I(t) = \tilde{I}_0 e^{i\omega t}$$

Since

$$I = -\frac{dQ}{dt}$$

$$Q = -\int I dt = -\frac{\tilde{I}_0}{i\omega} e^{i\omega t}$$

we have

$$\frac{\tilde{I}_0}{i\omega C} e^{i\omega t} + R\tilde{I}_0 e^{i\omega t} = \mathcal{E}_0 e^{i\omega t}$$

Canceling the  $e^{i\omega t}$ , we get


$$\tilde{I}_0 = \frac{\mathcal{E}_0}{\frac{1}{i\omega C} + R} = \frac{\mathcal{E}_0}{R^2 + (1/\omega C)^2} \left( R + i\frac{1}{\omega C} \right) = \frac{\mathcal{E}_0}{\sqrt{R^2 + (1/\omega C)^2}} e^{i\phi}$$

$$\tan \phi = \frac{1/\omega C}{R} = \frac{1}{R\omega C}$$

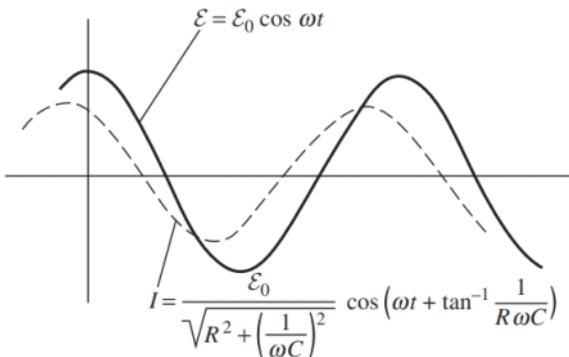(2) Thus, we obtain

$$\mathcal{E} = \mathcal{E}_0 e^{i\omega t}$$

$$I = \frac{\mathcal{E}_0}{\sqrt{R^2 + (1/\omega C)^2}} e^{i\left(\omega t + \tan^{-1} \frac{1}{R\omega C}\right)}$$




The maximum in  $I$  occurs here a little earlier than the maximum in  $\mathcal{E}$ .

## C. RLC CIRCUIT

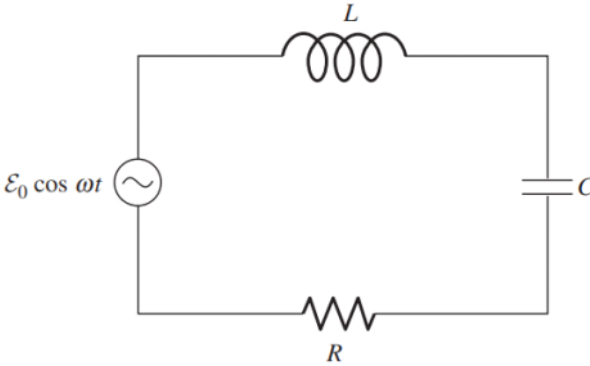(1) The RLC circuit driven by a sinusoidal electromotive force where we

have defined  $Q$  to be the charge on the bottom plate of the capacitor.



The Kirchoff loop equation for the series RLC circuit is

$$L \frac{dI}{dt} - \frac{Q}{C} + RI = \mathcal{E}_0 e^{i\omega t}$$

$$I(t) = \tilde{I}_0 e^{i\omega t} \text{ where } \tilde{I}_0 \text{ is a complex number}$$

$$Q = - \int I dt = - \frac{\tilde{I}_0}{i\omega} e^{i\omega t}$$

Thus, we obtain

$$i\omega L \tilde{I}_0 e^{i\omega t} + \frac{\tilde{I}_0}{i\omega C} e^{i\omega t} + R \tilde{I}_0 e^{i\omega t} = \mathcal{E}_0 e^{i\omega t}$$

Canceling the  $e^{i\omega t}$ , we get

$$i\omega L \tilde{I}_0 + \frac{\tilde{I}_0}{i\omega C} + R \tilde{I}_0 = \mathcal{E}_0$$

$$\tilde{I}_0 = \frac{\mathcal{E}_0}{i\omega L + R + \frac{1}{i\omega C}}$$

$$= \frac{\mathcal{E}_0}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} \left( R - i \left( \omega L - \frac{1}{\omega C} \right) \right)$$

$$= \frac{\mathcal{E}_0}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} e^{i\phi}$$

$$= \frac{\mathcal{E}_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} e^{i\phi}$$

$$\tan \phi = \frac{\frac{1}{\omega C} - \omega L}{R} = \frac{1}{R\omega C} - \frac{\omega L}{R}$$

(2) Thus, we obtain


$$\mathcal{E} = \mathcal{E}_0 e^{i\omega t}$$

$$I = \frac{\mathcal{E}_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} e^{i\left(\omega t + \tan^{-1}\left(\frac{1}{R\omega C} - \frac{\omega L}{R}\right)\right)}$$

## 8-2 Resonant Circuit

### A. RLC CIRCUIT

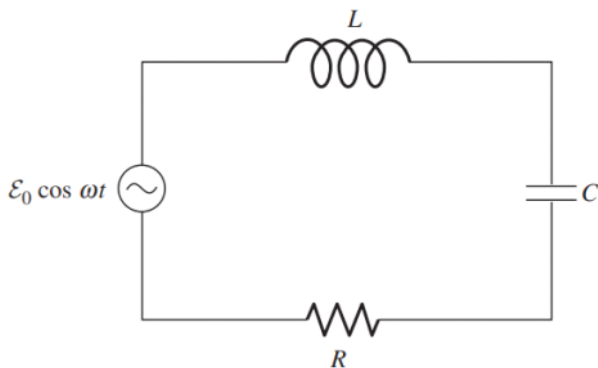- (1) The RLC circuit driven by a sinusoidal electromotive force.




We have

$$\mathcal{E} = \mathcal{E}_0 e^{i\omega t}$$
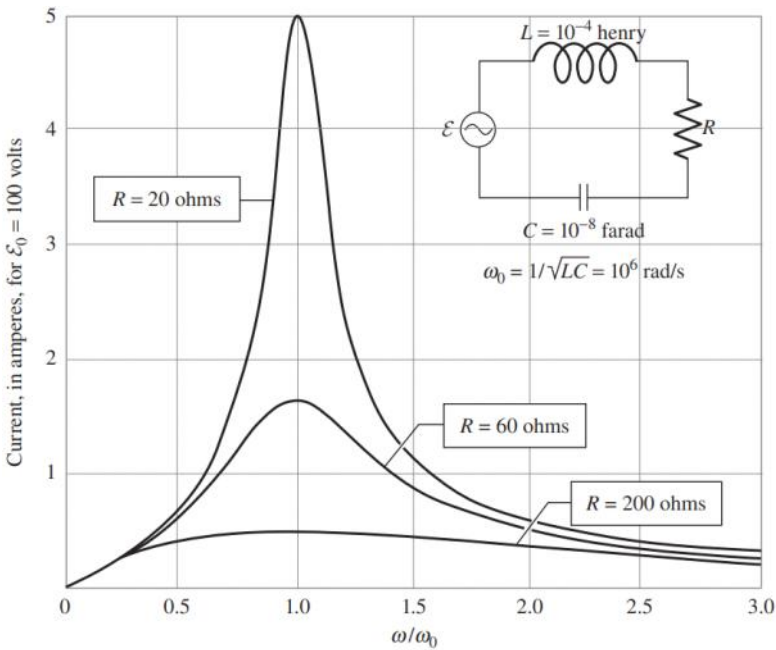
$$I = \frac{\mathcal{E}_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} e^{i\left(\omega t + \tan^{-1}\left(\frac{1}{R\omega C} - \frac{\omega L}{R}\right)\right)}$$





- (2) The maximum in  $I_0(\omega)$  occurs at

$$\omega L - \frac{1}{\omega C} = 0 \Rightarrow \omega^2 = \frac{1}{LC} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

Thus, we obtain

$$\begin{aligned} \mathcal{E}_{\max} &= \mathcal{E}_0 \\ I_{0,\max} &= \frac{\mathcal{E}_0}{\sqrt{R^2 + 0^2}} = \frac{\mathcal{E}_0}{R} \end{aligned}$$

- (3) Width of the  $I_0(\omega)$  curve

The width of a resonance peak is the full width,  $2\Delta\omega$ , between half-power points, i.e.,

$$P_{1/2} = \frac{1}{2} P_{\max}$$

Since

$$P = I^2 R$$

we obtain

$$\begin{aligned} I_{0,1/2} &= \frac{1}{\sqrt{2}} I_{0,\max} = \frac{\mathcal{E}_0}{\sqrt{R^2 + R^2}} \\ \Rightarrow \left| \omega L - \frac{1}{\omega C} \right| &= R \end{aligned}$$

Consider frequencies in the neighborhood of  $\omega_0$ ,

$$\omega = \omega_0 + \Delta\omega = \omega_0 \left( 1 + \frac{\Delta\omega}{\omega_0} \right)$$

To first order in  $\Delta\omega/\omega_0$ ,

$$\begin{aligned} \omega L - \frac{1}{\omega C} &= \omega_0 L \left( 1 + \frac{\Delta\omega}{\omega_0} \right) - \frac{1}{\omega_0 C \left( 1 + \frac{\Delta\omega}{\omega_0} \right)} \\ &\approx \omega_0 L \left( 1 + \frac{\Delta\omega}{\omega_0} \right) - \frac{1}{\omega_0 C} \left( 1 - \frac{\Delta\omega}{\omega_0} \right) \end{aligned}$$

Since


$$\omega_0^2 = \frac{1}{LC} \Rightarrow \omega_0 L = \frac{1}{\omega_0 C}$$

thus, we obtain

$$\begin{aligned} \omega L - \frac{1}{\omega C} &= \omega_0 L \left( 1 + \frac{\Delta\omega}{\omega_0} \right) - \omega_0 L \left( 1 - \frac{\Delta\omega}{\omega_0} \right) = \omega_0 L \frac{2\Delta\omega}{\omega_0} = R \\ \Rightarrow \frac{2|\Delta\omega|}{\omega_0} &= \frac{R}{\omega_0 L} = R\omega_0 C \end{aligned}$$

## B. DAMPED OSCILLATOR CIRCUIT

(1) A series RLC circuit.

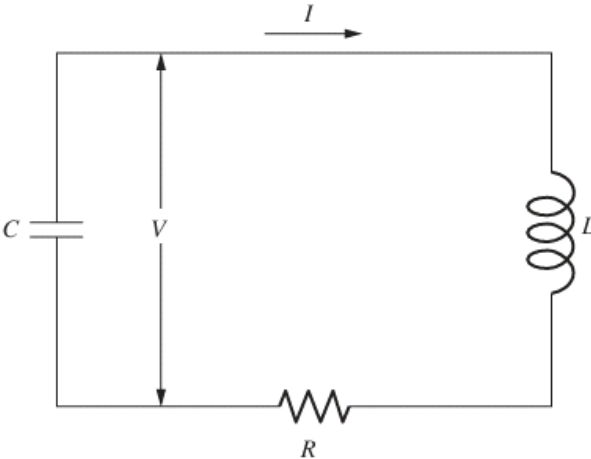

$$L \frac{dI}{dt} + RI - \frac{Q}{C} = 0$$

$$Q = CV$$

$$I = -\frac{dQ}{dt} = -C \frac{dV}{dt}$$

Thus, we have

$$L \frac{d}{dt} \left( -C \frac{dV}{dt} \right) + R \left( -C \frac{dV}{dt} \right) - V = 0$$
$$\frac{d^2V}{dt^2} + \frac{R}{L} \frac{dV}{dt} + \frac{1}{LC} V = 0$$

This is a damped oscillation equation. We shall try a solution of the form

$$V(t) = Ae^{-\alpha t} e^{i\omega t}$$

Since

$$\frac{dV}{dt} = Ae^{-\alpha t} e^{i\omega t} (-\alpha + i\omega)$$
$$\frac{d^2V}{dt^2} = Ae^{-\alpha t} e^{i\omega t} (\alpha^2 - 2i\alpha\omega - \omega^2)$$

thus, we obtain

$$Ae^{-\alpha t} e^{i\omega t} (\alpha^2 - 2i\alpha\omega - \omega^2) + \frac{R}{L} Ae^{-\alpha t} e^{i\omega t} (-\alpha + i\omega) + \frac{1}{LC} Ae^{-\alpha t} e^{i\omega t} = 0$$

$$(\alpha^2 - 2i\alpha\omega - \omega^2) + \frac{R}{L} (-\alpha + i\omega) + \frac{1}{LC} = 0$$

$$\alpha^2 - \omega^2 - \alpha \frac{R}{L} + \frac{1}{LC} - i \left( 2\alpha\omega - \frac{R\omega}{L} \right) = 0$$

We require


$$2\alpha\omega - \frac{R\omega}{L} = 0 \Rightarrow \alpha = \frac{R}{2L}$$

$$\alpha^2 - \omega^2 - \alpha \frac{R}{L} + \frac{1}{LC} = 0 \Rightarrow \omega^2 = \frac{1}{LC} - \frac{R^2}{4L^2}$$

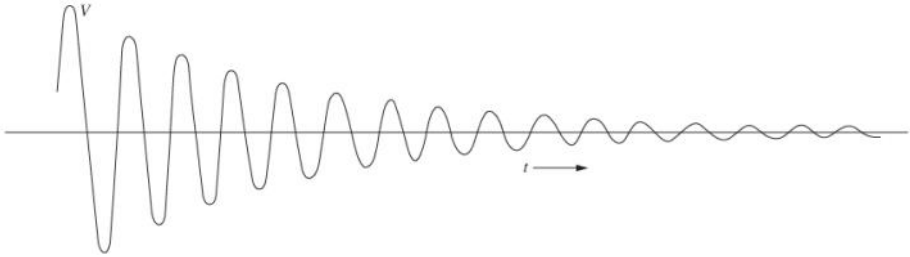
(2) Thus, we obtain

$$V(t) = Ae^{-\frac{R}{2L}t} e^{i\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}t}$$

$$\begin{aligned}
I &= -C \frac{dV}{dt} \\
&= ACe^{-\alpha t} e^{i\omega t} (\alpha - i\omega) \\
&= ACe^{-\alpha t} \sqrt{\alpha^2 + \omega^2} e^{i(\omega t - \tan^{-1} \omega/\alpha)} \\
&= ACe^{-\frac{R}{2L}t} \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC} - \frac{R^2}{4L^2}} e^{i\left(\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}t - \tan^{-1} \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} / \frac{R}{2L}\right)} \\
&= A \sqrt{\frac{C}{L}} e^{-\frac{R}{2L}t} e^{i\left(\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}t - \tan^{-1} \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} / \frac{R}{2L}\right)}
\end{aligned}$$



Zoom in a period:

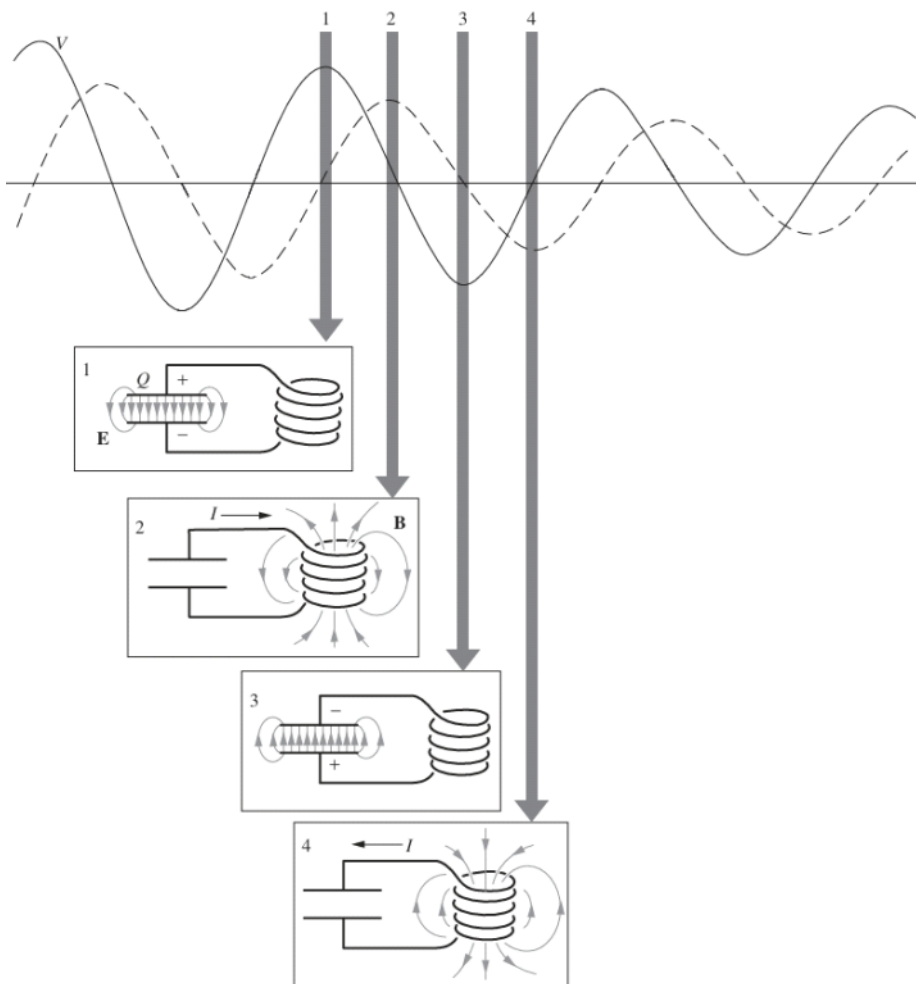

(3) If  $R = 0$ ,

$$V(t) = Ae^{-\frac{0}{2L}t} e^{i\sqrt{\frac{1}{LC} - \frac{0}{4L^2}}t} = Ae^{i\omega_0 t} \text{ where } \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\begin{aligned}
I(t) &= A \sqrt{\frac{C}{L}} e^{-\frac{0}{2L}t} e^{i\left(\sqrt{\frac{1}{LC} - \frac{0}{4L^2}}t - \tan^{-1} \sqrt{\frac{1}{LC} - \frac{0}{4L^2}} / \frac{0}{2L}\right)} \\
&= A \sqrt{\frac{C}{L}} e^{i\left(\sqrt{\frac{1}{LC}}t - \tan^{-1} \infty\right)} \\
&= A \sqrt{\frac{C}{L}} e^{i(\omega_0 t - \pi/2)}
\end{aligned}$$


we obtain a undamped oscillator.

(4) If  $\frac{1}{LC} - \frac{R^2}{4L^2} = 0 \Rightarrow R = 2\sqrt{\frac{L}{C}}$ ,

$$V(t) = A e^{-\frac{R}{2L}t} e^{i0t} = A e^{-\frac{1}{\sqrt{LC}}t} = A e^{-\omega_0 t}$$

$$I(t) = A \sqrt{\frac{C}{L}} e^{-\frac{R}{2L}t} e^{i\left(0t - \tan^{-1} 0 / \frac{R}{2L}\right)} = A \sqrt{\frac{C}{L}} e^{-\frac{R}{2L}t} = A \sqrt{\frac{C}{L}} e^{-\omega_0 t}$$


we obtain the critical damping.

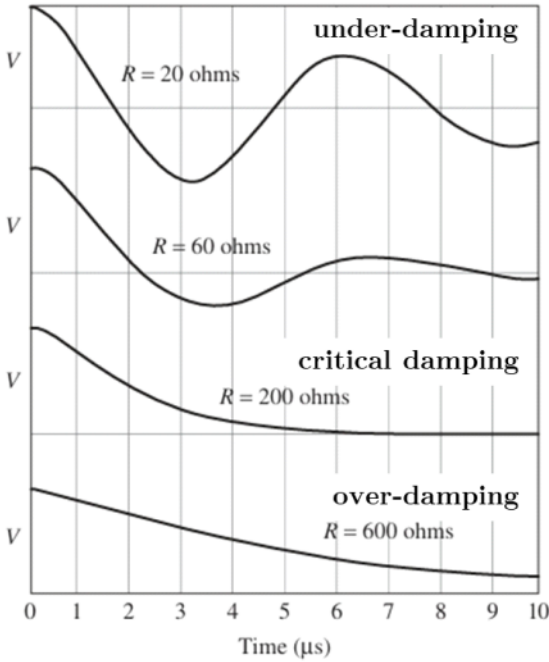

# 8-3 Power and Energy in Alternating-Current Circuits

## A. ADMITTANCE AND IMPEDENCE

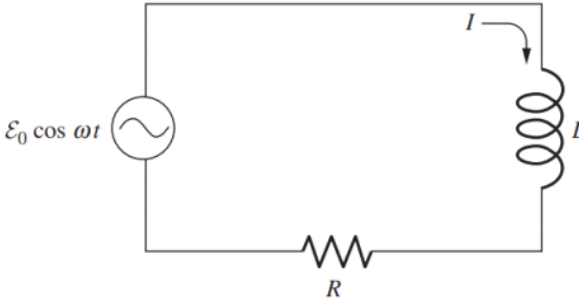- (1) The relation between current flow in a circuit element and the voltage across the element can be expressed as a relation between the complex numbers that represent the voltage and the current.



The voltage and current oscillation are represented by

$$\tilde{V} = \mathcal{E}_0 e^{i\omega t}$$

$$\tilde{I} = \frac{\mathcal{E}_0}{\sqrt{R^2 + (\omega L)^2}} e^{i(\omega t + \phi)} = \frac{e^{i\phi}}{\sqrt{R^2 + (\omega L)^2}} \mathcal{E}_0 e^{i\omega t}$$

$$\phi = -\tan^{-1}\left(\frac{\omega L}{R}\right)$$

- (2) We define a complex number as follows,

$$\tilde{I} = Y \tilde{V}$$

$$Y = \frac{e^{i\phi}}{\sqrt{R^2 + (\omega L)^2}} \cdots \text{admittance (conductivity in complex)}$$

$$= \frac{1}{i\omega L + R}$$

The same relation can be expressed with the reciprocal of  $Y$ , denoted by  $Z$ ,


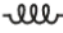

$$\tilde{V} = Z \tilde{I}$$

$$Z = \frac{1}{Y} \cdots \text{impedance (resistivity in complex)}$$

- (3) The properties of the three basic circuit elements are summarized




## Complex impedances

Symbol	Admittance, $Y$	Impedance, $Z = 1/Y$
$R$ 	$\frac{1}{R}$	$R$
$L$ 	$\frac{1}{i\omega L}$	$i\omega L$
$C$ 	$i\omega C$	$\frac{1}{i\omega C}$
	$I = YV$	$V = ZI$
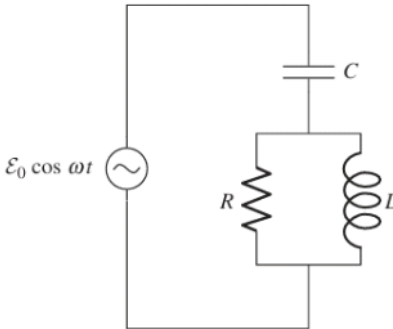
### EXAMPLES:

- Find the complex voltage across, and current through, each of the three elements where  $L = R/\omega$  and  $C = 1/\omega R$ .



### ANSWER:

The three impedances are then

$$Z_C = \frac{1}{i\omega C} = -iR$$

$$Z_R = R$$

$$Z_L = i\omega L = iR$$

The impedance of the entire circuit is

$$Z = Z_C + \frac{1}{\frac{1}{Z_R} + \frac{1}{Z_L}} = \frac{1}{i\omega C} + \frac{1}{\frac{1}{R} + \frac{1}{i\omega L}} = -iR + \frac{1}{\frac{1}{R} + \frac{1}{iR}} = R \frac{1-i}{2}$$

The complex total current:

$$\tilde{V}_\mathcal{E} = Z\tilde{I} \Rightarrow \tilde{I} = \frac{\mathcal{E}_0}{Z} = \frac{\mathcal{E}_0}{R} \frac{1}{1-i} = \frac{\mathcal{E}_0}{R} (1+i)$$

The complex voltage across each element:

$$\tilde{V}_C = Z_C \tilde{I} = (-iR) \frac{\mathcal{E}_0}{R} (1+i) = \mathcal{E}_0 (1-i)$$

$$\tilde{V}_R = \tilde{V}_L = \mathcal{E}_0 - \tilde{V}_C = \mathcal{E}_0 - \mathcal{E}_0 (1-i) = i\mathcal{E}_0$$

The complex current through each element:

$$\begin{aligned}\tilde{I}_C &= \tilde{I} \\ \tilde{I}_R &= \frac{\tilde{V}_R}{Z_R} = \frac{i\mathcal{E}_0}{R} \\ \tilde{I}_L &= \frac{\tilde{V}_L}{Z_L} = \frac{i\mathcal{E}_0}{iR} = \frac{\mathcal{E}_0}{R}\end{aligned}$$

## B. POWER AND ENERGY IN ALTERNATING-CURRENT CIRCUITS

(1) The energy dissipated in the resistor is given by

$$P_R = RI^2 = \frac{V^2}{R}$$

However, as  $I = \tilde{I}_0 e^{i\omega t}$  and  $V = V_0 e^{i\omega t}$ , we shall evaluate the average power instead of the instantaneous power.

Since

$$\overline{V^2} = \overline{(VV)} = \Re \frac{1}{2} VV^* = \Re \frac{1}{2} V_0 e^{i\omega t} V_0 e^{-i\omega t} = \frac{V_0^2}{2}$$

or take the real part only


$$\frac{V_0^2}{T} \int_0^T \cos^2 \omega t \, dt = \frac{V_0^2}{T} \int_0^T \left( \frac{1}{2} + \frac{1}{2} \cos 2\omega t \right) dt = \frac{V_0^2}{2T} T = \frac{V_0^2}{2}$$

The average power dissipated in the resistor is

$$\bar{P}_R = \frac{1}{2} \frac{V_0^2}{R} = \frac{V_{\text{rms}}^2}{R}$$

where
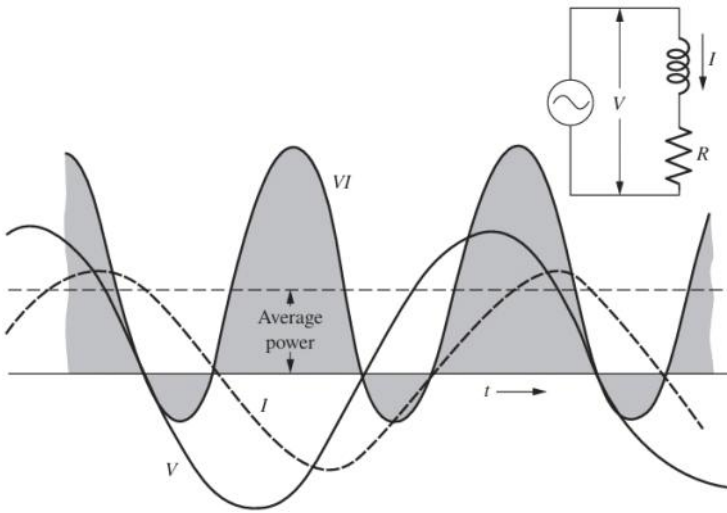
$$V_{\text{rms}} = \frac{V_0}{\sqrt{2}} \cdots \cdots \text{root-mean-square (rms) value}$$



- (2) The average power  $\bar{P}$  delivered to the RL circuit corresponds to the horizontal dashed line.

$$VI = V_0 e^{i\omega t} \tilde{I}_0 e^{i\omega t} = V_0 \tilde{I}_0 e^{2i\omega t}$$

$$\bar{P} = \overline{(VI)} = \Re \frac{1}{2} V_0 \tilde{I}_0^* e^{i\omega t} e^{-i\omega t} = \frac{1}{2} V_0 I_0 \cos \phi = V_{\text{rms}} I_{\text{rms}} \cos \phi$$